

# DLD Assignment 6

Balaji

January 2021

## 1 Boolean Equation

$$g = B'C'D' + ABCD' \quad (1)$$

## 2 Logic Gate Circuit

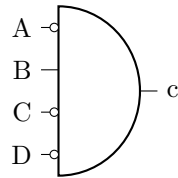


Figure 1: Logic Gate for 2.5.1 (g)